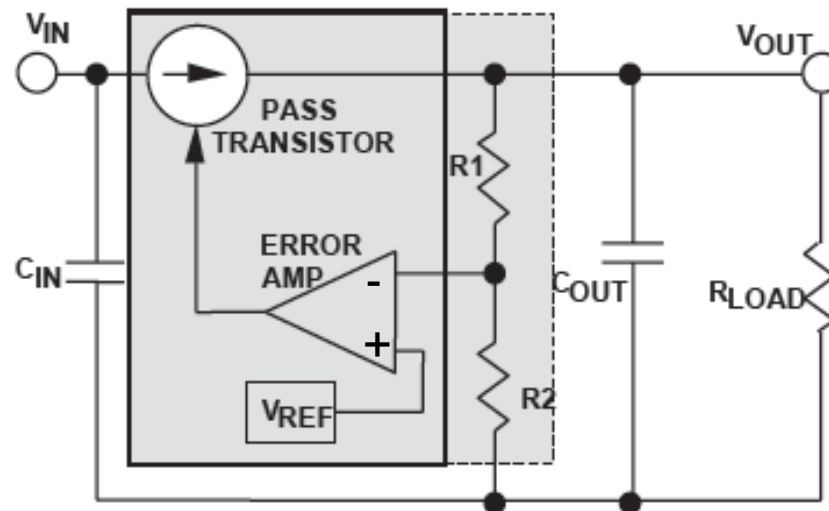


# 线性稳压器 基础知识

# 什么是线性稳压器 (Linear Regulator)

- 线性稳压器通过一个通流器件（通常为晶体管或MOSFET）承受不需要的电压，从而使输入电压保持恒定。
- 通流器件的特性类似于一个可调电阻。



# 线性稳压器的优缺点

## 优点


- 低输出纹波，低噪声，EMI辐射小
- 成本低（在小功率时）
- 结构简单，只需少数几个外围元件，容易调试和设计
- 暂态响应快
- 短路保护容易设计

## 缺点

- 效率低，能量以热能的形式消耗，当  $V_{in}$  和  $V_{out}$  相差较大时尤为突出
- 散热要求高，功率越大，或  $V_{in}$  和  $V_{out}$  相差越大，线性稳压器产生的热损耗越大
- 只能降压

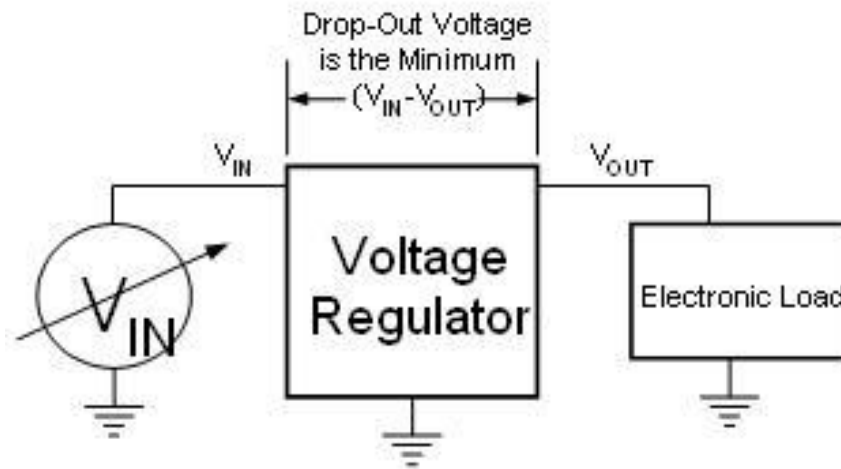
# 线性稳压器的最小压差 (dropout voltage)

- 线性稳压器为了维持正常工作,  $V_{in}$  和  $V_{out}$  之间必须有一个差值, 此差值的最小值称为线性稳压器的最小压差 (dropout voltage)



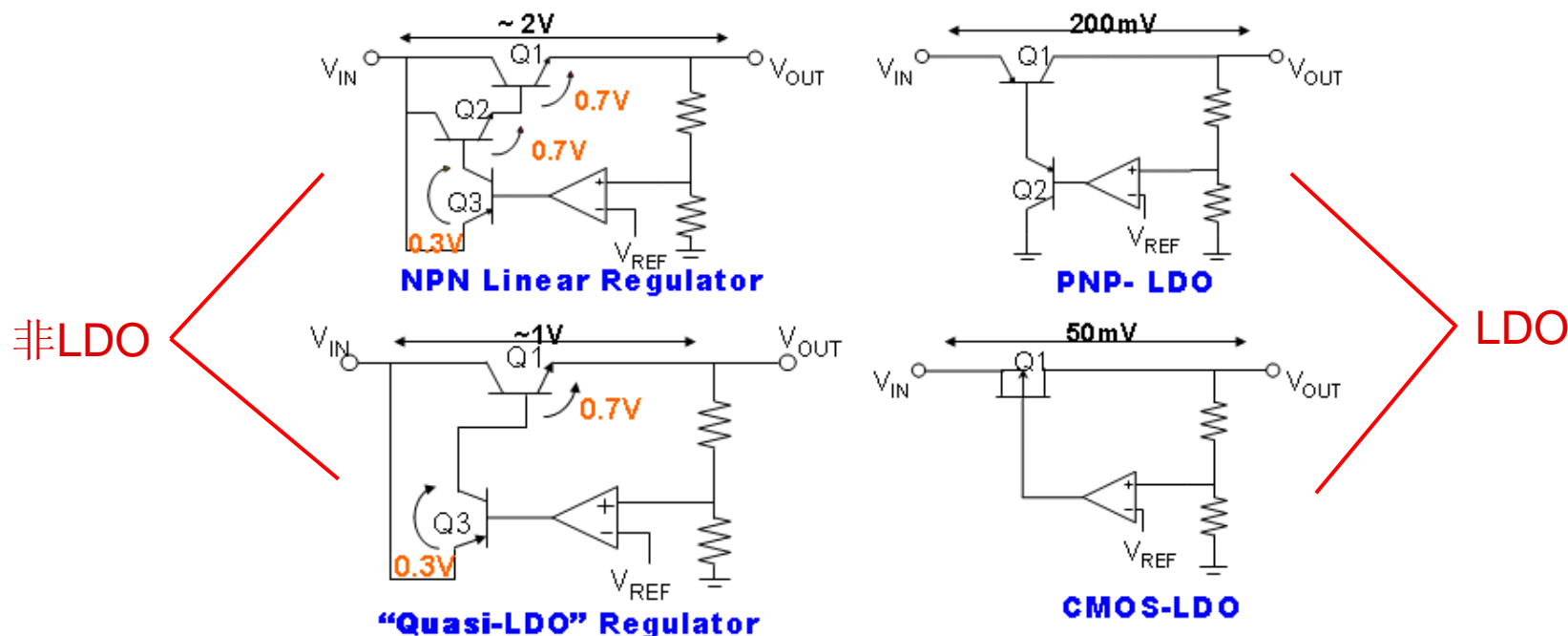
# 线性稳压器的类型

- 线性稳压器的通流器件可以是晶体管或者MOSFET，不同的通流器件有不同的最小压差特性。
  - NPN型：最小压差较大，一般在2V以上。如7805，LM317。
  - “准LDO”型：最小压差比NPN型小，但仍在1V以上。如LM1117。
  - PNP型：最小压差较小，但对输出电容ESR有要求。如TPS7A4901。
  - MOSFET型：最小压差很小，PMOS型对输出电容ESR有要求。如TPS7A8300。
- 最小压差很小的线性稳压器称为LDO(low drop-out linear regulator)


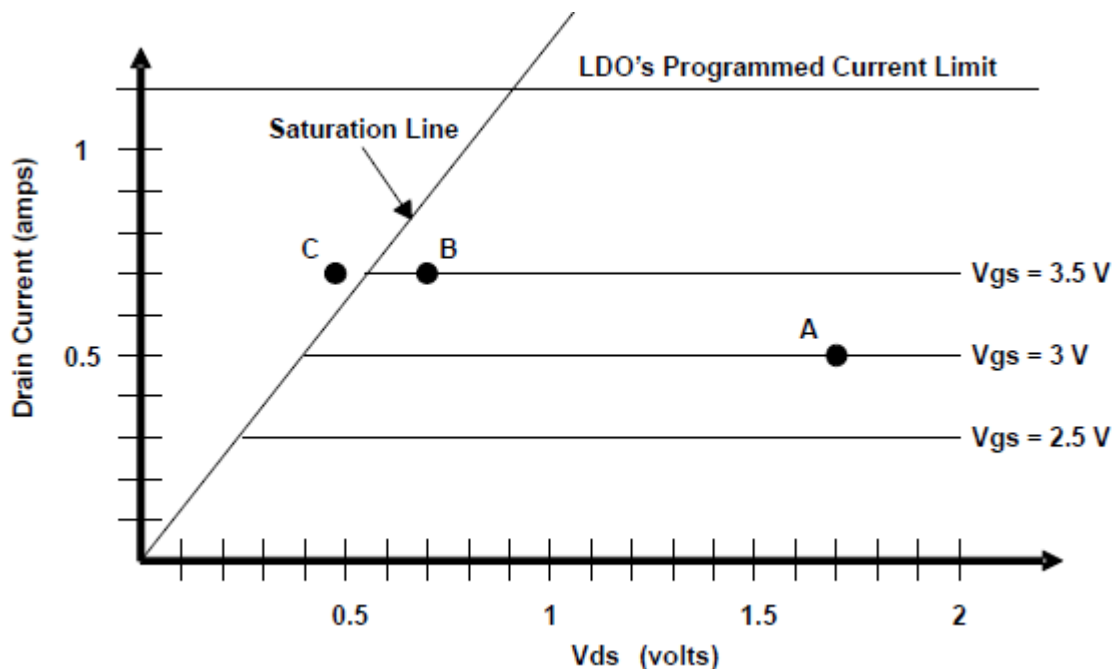
# 理解Dropout

- 为维持输出电流，线性稳压器必须工作在线性区。当 $V_{DS}$ 下降到一定程度时，线性稳压器会进入饱和区，导致电流下降。
- 例如 $V_{in}=5V$ ,  $V_{out}=3.3V$ ,  $I_{out}=500mA$ 时，线性稳压器工作在A点。若输入电压持续下降，会导致FET饱和，线性区与饱和区的临界点就是dropout电压。



# 抢答: TPS7A4901的Dropout Voltage?

$V_{DO}$	Dropout voltage	$V_{IN} = 95\% V_{OUT(nom)}, I_{OUT} = 100\text{ mA}$	260		mV
		$V_{IN} = 95\% V_{OUT(nom)}, I_{OUT} = 150\text{ mA}$	333	600	mV

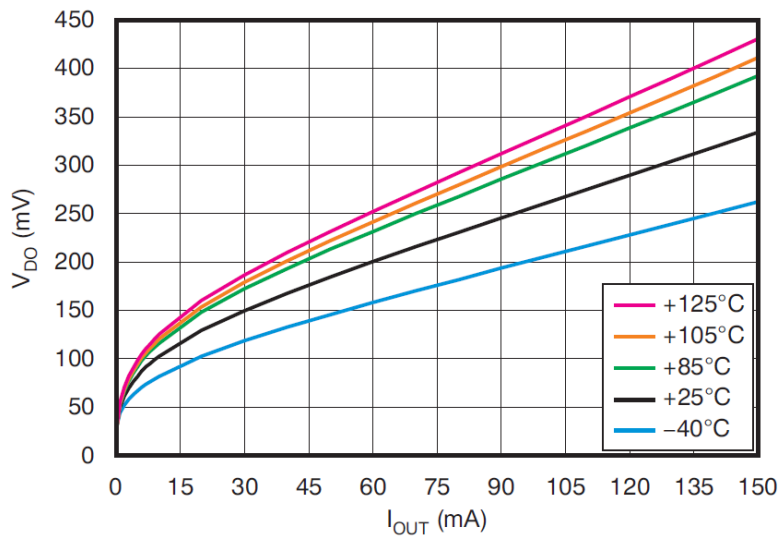


Figure 9. Dropout Voltage vs Output Current



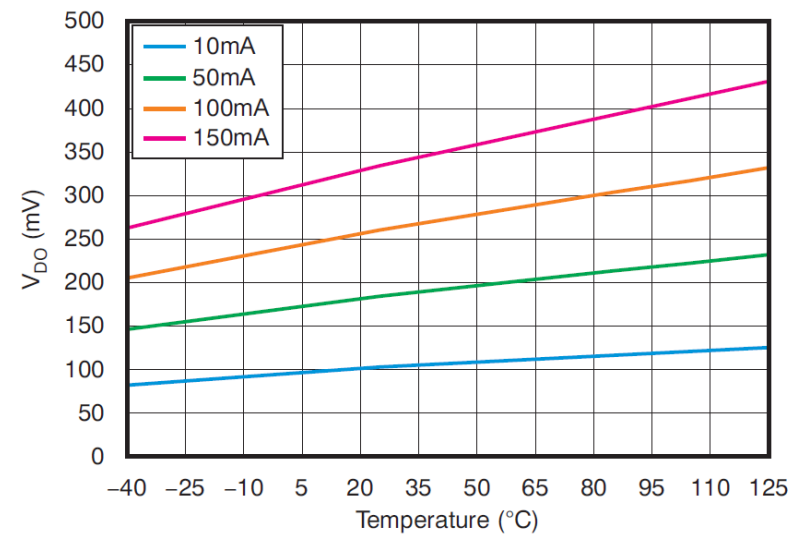


Figure 10. Dropout Voltage vs Temperature
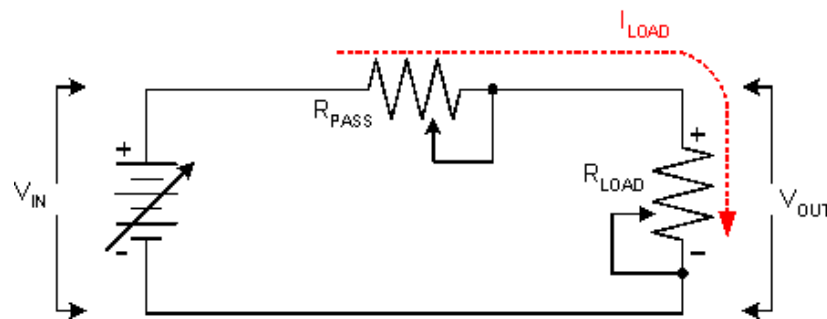
# 线性稳压器的简化模型(Simple Model)


- A basic (first order) linear voltage regulator can be modeled with two resistors and a power supply for  $V_{IN}$ .
- In reality, the only constant is the output voltage,  $V_{OUT}$ . Everything else can, and will, be constantly changing.
- The input voltage may have changes due to outside influences, the load current may change due to a dynamic change in the behavior of the load.
- Changes in these variables can all happen simultaneously, and the value needed for  $R_{PASS}$  to hold  $V_{OUT}$  at a constant value will need to change as well.



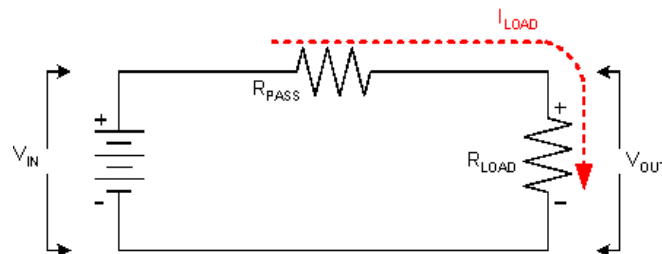

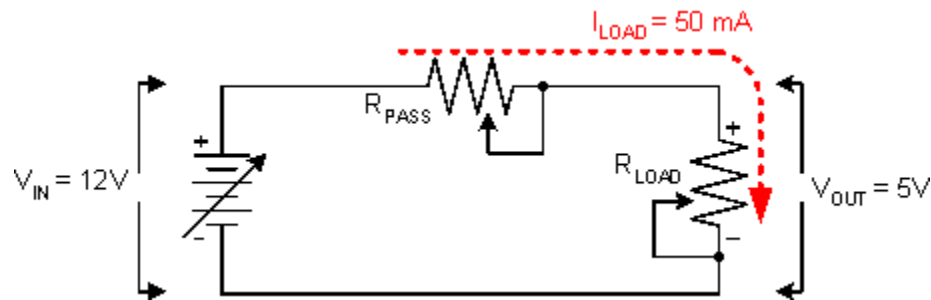
# Simple Model with Values

- For the first example, we will assign typical operating values and calculate the value needed for the series pass element  $R_{\text{PASS}}$ .
  - $V_{\text{IN}} = 12\text{V}$
  - $V_{\text{OUT}} = 5\text{V}$
  - $I_{\text{LOAD}} = 50\text{ mA}$
- With  $V_{\text{IN}} = 12\text{V}$  and  $V_{\text{OUT}} = 5\text{V}$ , the voltage across  $R_{\text{PASS}} = (12\text{V} - 5\text{V}) = 7\text{V}$
- With the current through  $R_{\text{PASS}} = I_{\text{LOAD}} = 50\text{ mA}$ , the needed resistance for  $R_{\text{PASS}} = (7\text{V} / 50\text{mA}) = 140\text{ Ohms}$



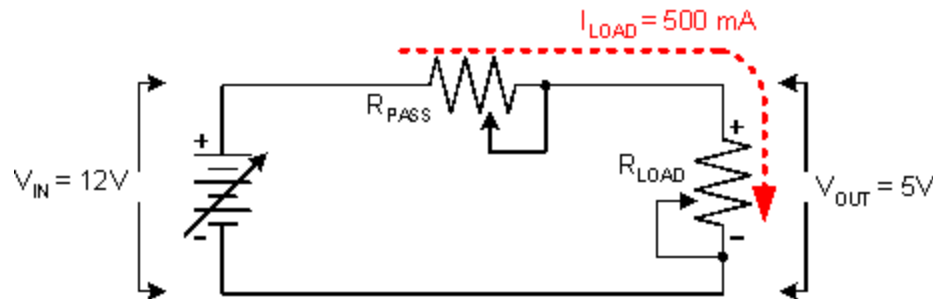
# Simple Model with Change of Load Current

- For the second example, we will change the load current from 50mA to 500mA and calculate the value needed for the series pass element  $R_{PASS}$ .
  - $V_{IN} = 12V$
  - $V_{OUT} = 5V$
  - $I_{LOAD} = 500\text{ mA}$
- With  $V_{IN} = 12V$  and  $V_{OUT} = 5V$ , the voltage across  $R_{PASS} = (12V - 5V) = 7V$
- With the current through  $R_{PASS} = I_{LOAD} = 500\text{ mA}$ , the needed resistance for  $R_{PASS} = (7V / 500mA) = 14\text{ Ohms}$


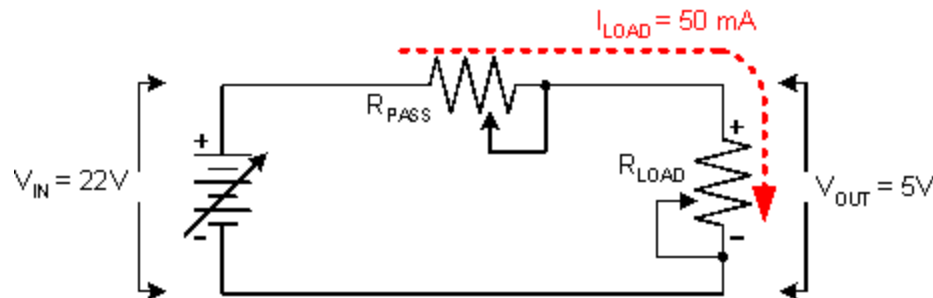
# Simple Model with Change in Input Voltage

- For the third example, we will change the input voltage from 12V to 22V and calculate the value needed for the series pass element  $R_{PASS}$ .
  - $V_{IN} = 22V$
  - $V_{OUT} = 5V$
  - $I_{LOAD} = 50\text{ mA}$
- With  $V_{IN} = 22V$  and  $V_{OUT} = 5V$ , the voltage across  $R_{PASS} = (22V - 5V) = 17V$
- With the current through  $R_{PASS} = I_{LOAD} = 50\text{ mA}$ , the needed resistance for  $R_{PASS} = (17V / 50mA) = 340\text{ Ohms}$



# The Control Loop


- It has been shown that the resistance of series pass element,  $R_{\text{PASS}}$ , needs to change as the operating conditions change.
- This is accomplished with a control loop.
- The error amplifier monitors the sampled output voltage, compares it to a known reference voltage, and actively changes  $R_{\text{PASS}}$  to keep  $V_{\text{OUT}}$  constant.
  - A characteristic of any linear voltage regulator is that it requires a finite amount of time to "correct" the output voltage after a change in load current demand.
  - This "time lag" defines the characteristic called transient response, which is a measure of how fast the regulator returns to steady-state conditions after a load change

暂态响应

# Simple Model, with Control Loop Blocks

- Here 'simple' blocks have added to show the four basic divisions of any linear voltage regulator:

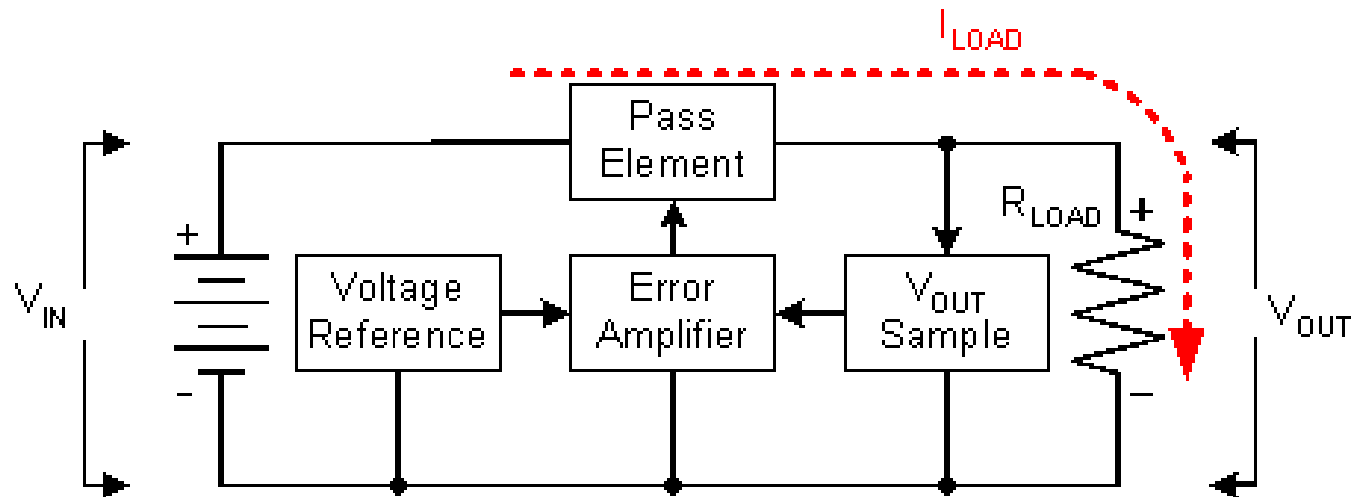- 1) Series Pass Element
- 2) Error Amplifier
- 3) VOUT Sampling Network
- 4) Reference Voltage



# 线性稳压器的其他关键性能指标

- 静态电流(Quiescent current): 空载时线性稳压器消耗的电流。
  - 静态电流是考察线性稳压器是否低功耗的重要指标, 在电池供电的应用中尤为关键。
- 电源抑制比(Power supply rejection ratio, 简称PSRR): 输出电压纹波和输入电压纹波的比值。
  - PSRR是考察线性稳压器抗噪性能的关键指标, 在对噪声要求较高的应用如音频, RF和无线中需要重点关注。
- 宽带噪声(Broadband noise): 规定频率范围的噪声总和。
  - 对于噪声要求较高的应用, 如PLL, RF和无线等, 需要重点注意。